

Name \_\_\_\_\_  
Regents Physics

---

## Series Circuit HW Problem

A circuit contains the following connected in series:

- A 120 V battery
- 100  $\Omega$  resistor
- A variable resistor
- A switch
- A 25  $\Omega$  lamp (lightbulb in other words)

### Step 1:

- Draw the circuit using the symbols from your reference tables.
- Show a voltmeter measuring the potential difference (voltage) across the lamp
- Show an ammeter measuring the current in the circuit

### Step 2:

- Determine to what resistance the variable resistor needs to be set to have a current of 0.4 A. Show all work below for credit.

### Step 3:

Determine the potential difference (voltage drop) across (show all work below)

- The lamp 100  $\Omega$  resistor
  
- The 25  $\Omega$  lamp
  
- The variable resistor

